



VIT[®]
Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Fall Semester 2021-2022

ECE5017 - Digital Design with FPGA ELA

M.Tech VLSI Design

School of Electronics Engineering

Vellore Institute of Technology

Name: Shreyas S Bagi

Register Number: 21MVD0086

Slot: L5+L6


Date:13/10/2021

Lab Task 02

Structural Modelling

Aim: Design a 16-bit ALU in structural modelling using Verilog HDL, which performs the following functions as shown in table. To test the ALU, write a Verilog test-bench code.

F2	F1	F0	FUNCTION
0	0	0	A+B
0	0	1	A+1
0	1	0	A-B
0	1	1	A-1
1	0	X	A*B

 

Objective:

- To design the ALU circuit using Verilog HDL.
- To write the test bench for generating stimulus.
- To perform functional simulation.
- Understand instantiation of gates, gate symbols, and truth tables.
- Design of ALU circuit using Structural Modelling.
-

Software Details:

For design Functional Simulation: Modelsim-INTEL FPGA STARTER EDITION.

Date:13/10/2021

Verilog Code :

// The Keywords of Verilog are highlighted in Bold.

```
`timescale 10ns/1ns

module alu_F(A,B,F,Y); // Module declaration for ALU

    parameter N=16; // Input lines A and B are of 16bit
    parameter C=3; // 3 bit select line

    input [N-1:0] A,B; // Input lines for ALU

    input [C-1:0] F; // Control lines for ALU or Selection of particular function.

// This can used as Control path line.

    output [(2*N)-1:0] Y; // 32-bit output line because of Multiplication operation.

    wire [(2*N)-1:0] I0, I1,I1B, I2, I3, I4,I5,I6,I7;

    wire F1_bar, F2_bar, F0_bar;

    not G1 (F2_bar, F[2]);
    not G2 (F1_bar, F[1]);
    not G3 (F0_bar, F[0]);

    assign I1B=16'b0000_0000_0000_0001; // Logic 1

// Adder module Instantiation

    add_alu G4 (I0,A,B);    // 000 ----- A+B

// Adder module Instantiation

    add_alu G5 (I1,A,I1B);  // 001 ----- A+1

// Subtraction module Instantiation

    sub_alu G6 (I2,A,B);    // 010 ----- A-B

// Subtraction module Instantiation

    sub_alu G7 (I3,A,I1B);  // 011 ----- A-1

// Multiplication module Instantiation

    mul_alu G8 (I4,A,B);    // 100 ----- A*B
    mul_alu G9 (I5,A,B);    // 101 ----- A*B

    mux_8_to_1 G10 (Y,I0,I1,I2,I3,I4,I5,I6,I7,F); // 8 to 1 MUX

endmodule
```

Date:13/10/2021

// Adder Module Declaration

module add_alu (Y,A,B);

parameter N=16;

input [N-1:0] A,B;

output [(2*N)-1:0] Y; // MSB bit is Carry and rest bits are Sum part

assign Y=A+B; // Dataflow modelling of Addition of inputs.

endmodule

// Subtraction Module

module sub_alu (Y,A,B);

parameter N=16;

input [N-1:0] A,B;

output [(2*N)-1:0] Y; // MSB bit is Borrow and rest are difference bits

assign Y=A-B; // Dataflow modelling of Subtraction of inputs.

endmodule

// Multiplication Module

module mul_alu (Y,A,B);

parameter N=16;

input [N-1:0] A,B;

output [(2*N)-1:0] Y;

assign Y=A*B; // Dataflow modelling of Multiplication of inputs.

endmodule

// Mux 2 to 1

module mux_2_to_1 (Y,I0,I1,Sel);

parameter N=32;

input [N-1:0] I0,I1;

input Sel;

output [N-1:0] Y;

Date:13/10/2021

```

wire [N-1:0] Y1,Y2;

not G4 (Sel_bar,Sel);

// The following of and gate primitive, or gate primitive are defined for 32bit
operation.

and G1[N-1:0] (Y1,I0,Sel_bar); // Input and output is of 32 bit.

and G2[N-1:0] (Y2,I1,Sel); // Input and output is of 32 bit.

or G3[N-1:0] (Y,Y1,Y2); // Input and output is of 32 bit.

endmodule


// Mux 4 to 1

module mux_4_to_1 (Y,I0,I1,I2,I3,Sel);

    parameter N=32;

    input [N-1:0] I0,I1,I2,I3;

    input [1:0] Sel;

    output tri [N-1:0] Y;

    wire [N-1:0] Iout1,Iout2;

    mux_2_to_1 G1 (Iout1,I0,I1,Sel[0]);

    mux_2_to_1 G2 (Iout2,I2,I3,Sel[0]);

    mux_2_to_1 G3 (Y,Iout1,Iout2,Sel[1]);

endmodule


// Mux 8 to 1

module mux_8_to_1 (Y,I0,I1,I2,I3,I4,I5,I6,I7,Sel);

    parameter N=32;

    input [N-1:0] I0,I1,I2,I3,I4,I5,I6,I7;

    input [2:0] Sel;

    output tri [N-1:0] Y;

    wire [N-1:0] Iout1,Iout2;

    mux_4_to_1 G1 (Iout1,I0,I1,I2,I3,Sel[1:0]);

    mux_4_to_1 G2 (Iout2,I4,I5,I6,I7,Sel[1:0]);

    mux_2_to_1 G3 (Y,Iout1,Iout2,Sel[2]);

```

Date:13/10/2021

endmodule

Testbench Code :

```
module test_alu();  
  parameter N=16;  
  reg [N-1:0] A,B;  
  wire [N:0] Y;  
  parameter C=3;  
  reg [C-1:0] F;  
  alu_F G11 (A,B,F,Y);  
  initial  
  begin  
    $monitor($time,"A=%b,B=%b,F=%b,Y=%b",A,B,F,Y);  
    #2 A=65000;B=500;F=0; // A+B  
    #2 A=6999;B=30;F=1;  // A+1  
    #2 A=50;B=40;F=2;    // A-B  
    #2 A=10;B=80;F=3;    // A-1  
    #2 A=80;B=200;F=4;   // A*B  
    #2 A=100;B=90;F=5;   // A*B  
    #2 A=100;B=450;F=6;  
    #2 A=98;B=1000;F=7;  
    #5 $stop;  
  end  
endmodule
```

Date:13/10/2021

Simulation Waveform :

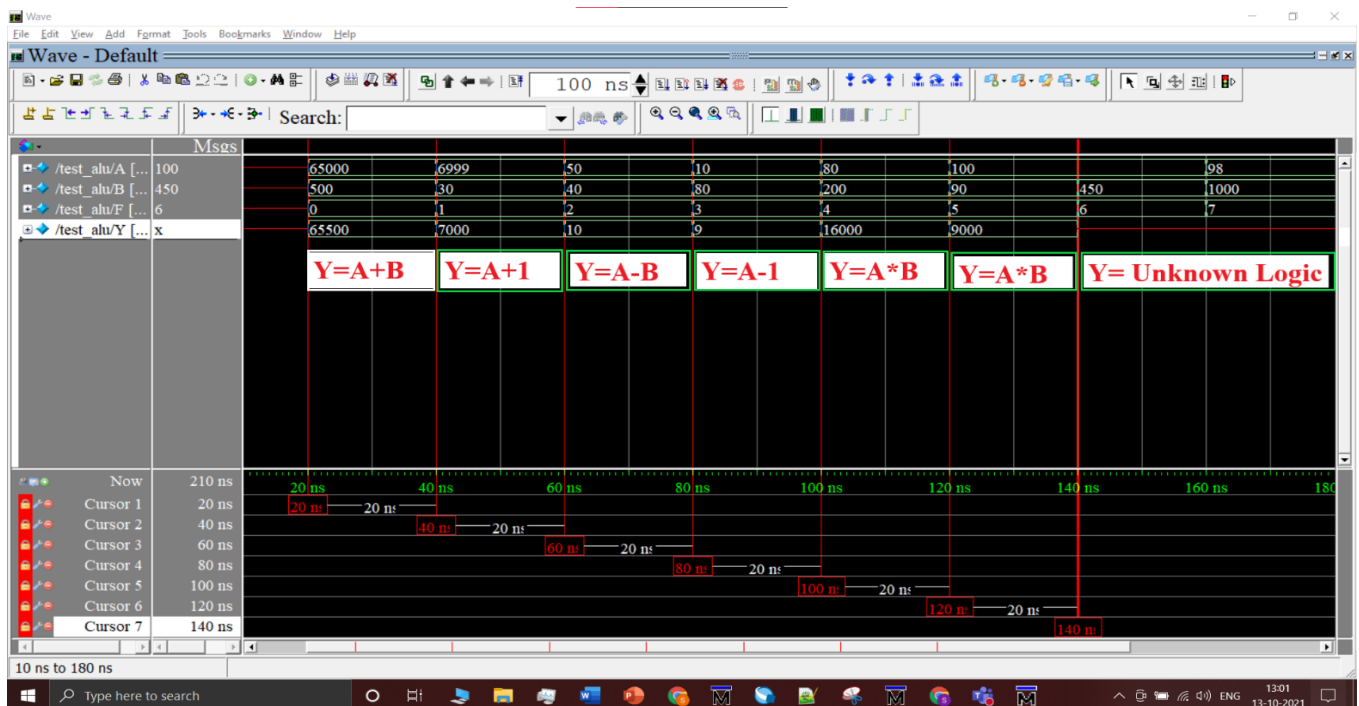


Figure 1.1 Simulation result for ALU Module for Different combination of A,B and Select lines.

In the Figure 1.1 we can observe when select line is 0 the operation performed is addition of A and B input. The addition output is observed from time 20ns to 40ns. Every time after 20ns the Inputs and Select line is getting updated. When Select line is 1 the operation performed is increment input A by one. The increment of Input A is observed from time 40ns to 60ns. When Select line is 2 the operation performed is subtraction of A and B input lines. The subtraction operation is observed from time 60ns to 80ns. When Select line is 3 the operation performed is decrement A by one. The decrement operation is observed from time 80ns to 100ns. When Select line is 4 and 5 the operation performed is multiplication of inputs. The Multiplication operation output can be observed from 100ns to 140ns. When Select line is 6 and 7 the output is at Unknown Logic because in the truth table there is function mentioned for these select lines.

Date:13/10/2021

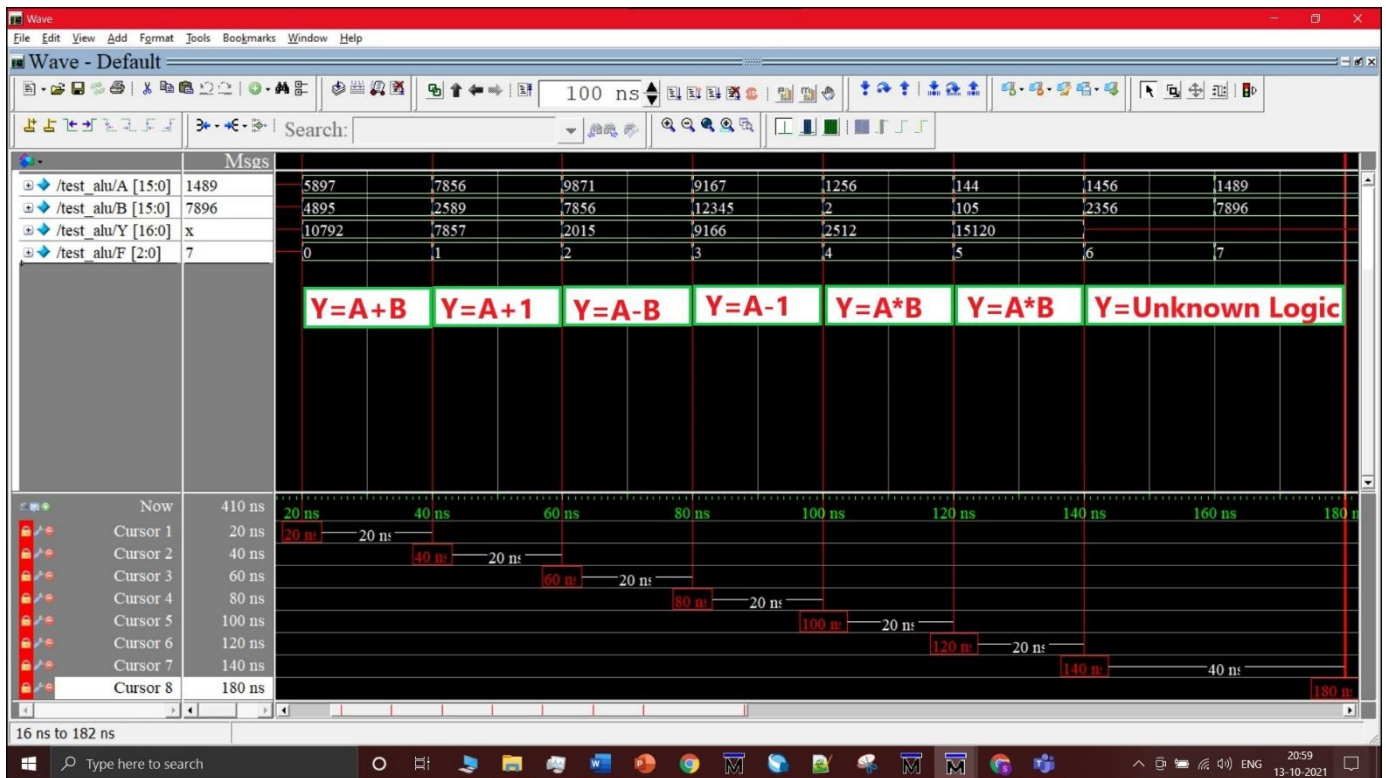


Figure 1.2 Simulation result for ALU Module for Different combination of A,B and Select lines.

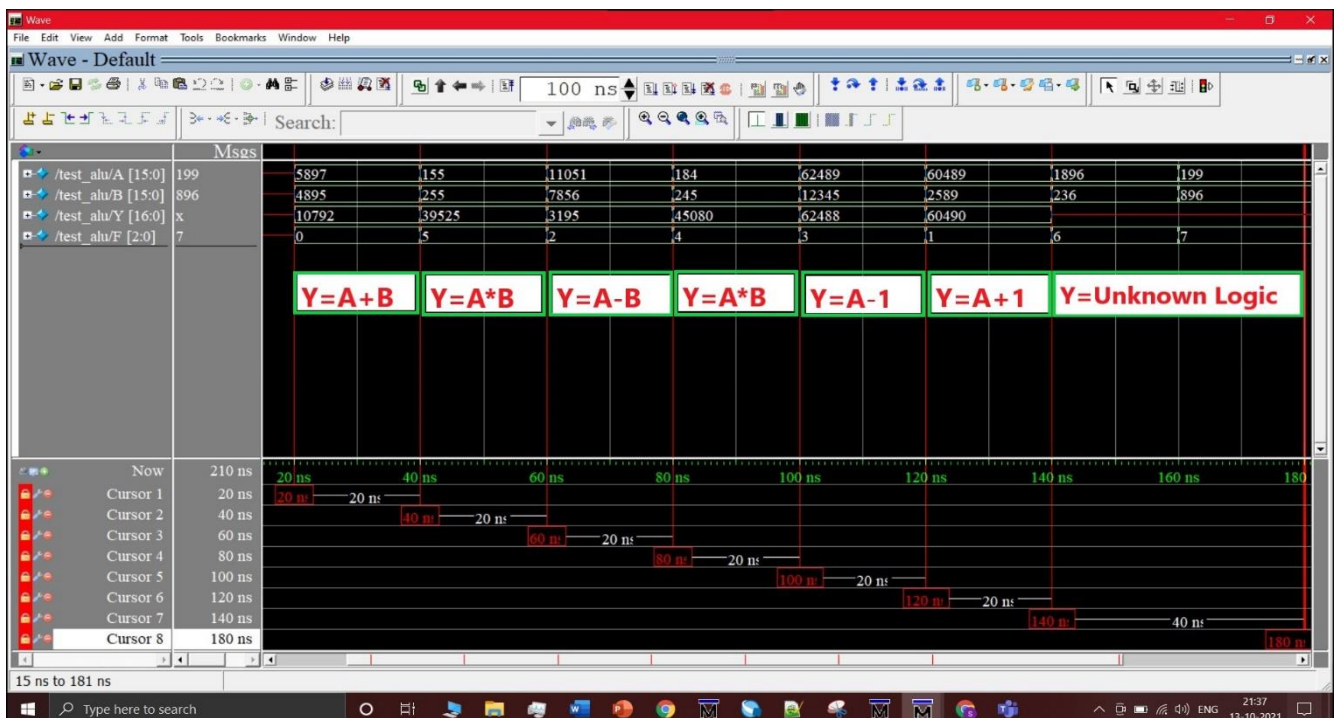


Figure 1.3 Simulation result for ALU Module for Different combination of A,B and Select lines.

Date:13/10/2021

Conclusion

Gate level modelling is a low level of abstraction. Design at this level is like describing a design in terms of a gate-level logic diagram.

Dataflow modelling is second highest level of abstraction. The module is implementing the function at a level of abstraction higher than gate level. It provides a powerful way to implement a design. Verilog allows a circuit to be designed in terms of data flow between registers and how a design processes data rather than instantiation of individual gates.

The Structural modelling is a combination of Gate level modelling and Dataflow modelling. In Structural style, a module is described as a set of interconnected components. The components can be modules, gate primitives and switch primitives.

Date:13/10/2021